

## **Simple Electricity**

Gears and Gadgets – Svoronos

### **Important Definitions**

**A/C** – Alternating Current (from wall, 120volts in the US)

**D/C** – Direct Current (from batteries, USB, 'wall wart' chargers, voltage varies)

**Positive (+)** – Point from where current flows

**Negative (-)** – Point to where electricity flows

**Ground (-)** or (green wire)

- in A/C applications, the third prong, or green wire
- in D/C applications, any point that connects to negative (-)

**Resistance** - (R) in formulas

- measured in Ohms (  $\Omega$  )
- the degree to which a substance opposes electric current

**Voltage** – ( V ) in formulas

- measured in Volts ( V )
- a measure of electromotive force

**Amperes** – ( I ) in formulas

- measured in amps (A -mostly A/C) and milliamps (mA -mostly D/C)
- the strength of electric current
- also measures the capacity of batteries in milliamp hours (mAh)

**Load** – the part of a circuit using the electricity. (LEDs, motors, etc.)

**Circuit** – an electrical application, where current moves from positive, through a load to negative or ground.

**Switch** – A device to control the flow of electric power. (On/Off or variable)

## **Alternating Current**

- Typically 110-120V
- Very dangerous
- There are no dedicated positive or negative wires. They both *alternate* from positive to negative 60 times a second (this alternating wave is measured in Hertz - Hz)
- Most large appliances run on A/C power

## **Direct Current**

- Voltage can range from miniscule (millivolts mV – one thousandth of a volt) to massive (Kilovolts kV – one thousand volts)
- for our purposes, we will use between 1.5-12V
- has dedicated Positive and Negative wires
- all portable electronics run on D/C power

## **Simple Circuits**


All circuits we will be working on will be D/C circuits; being safer, easier to work with and lower voltage (meaning less power to shock you)

All circuits require 3 basic components:

1. Positive and negative voltage ( wires on battery holders )
2. A load to run the power through (that is properly rated for the voltage provided)
3. An unbroken conduit to direct the power from positive to negative (wires, circuit boards, switches)

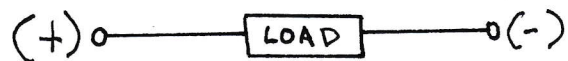
## **The Simplest Circuit**

Power travels from + to -  
through a load.


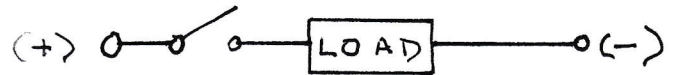
### Simple with Switch

Same configuration, however now a switch interferes with the flow of current. Switch can be placed either before or after the load.



### Loads in series (Series Circuit)

Loads can be configured in *Series*- from one to the next, where power flows through one to reach the next.


**The voltage needed to power the circuit is the sum of the voltage necessary to run each load.** i.e. Two 1.5v LEDs wired in series, require 3v to power.


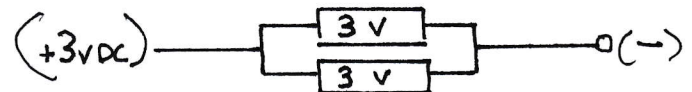
### Loads in parallel (Parallel Circuit)

*Parallel* circuits provides power to to multiple loads, independent of each other. Power does not have to flow through one to reach the next.

**The voltage needed remains the same** for each load. i.e. Two 1.5v LEDs, only require 1.5v when wired in parallel.



## Batteries in Series and Parallel

Batteries, like loads, can be connected in series or parallel to manipulate their output voltage and amperage.


**\*Every battery has a positive and negative terminal (+ is the 'button top' of AA batteries, - is the flat end. )\***

### Series Batteries

Batteries connected in series, have their voltages *added together*. While the amperage *remains the same*.

To connect batteries in series; link the battery terminals positive to negative, positive to negative, and so on until the desired voltage is reached.

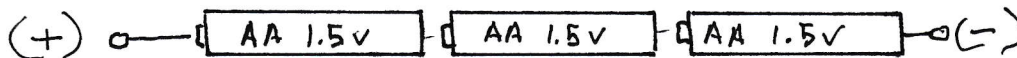Example: three AA batteries (1.5v each, 1000mA) connected in series, will produce a total voltage of 4.5v at 1000mA.



### Parallel Batteries

Batteries connected in parallel, *remain the same voltage, but add their amperages*.

To connect batteries in parallel; link all the positive terminals together to form one positive connection, then to the same with the negative terminals.

Example: three AA batteries (1.5v each) connected in parallel, will still output 1.5v, but at 3000mA.

